

4.3 DC motor control with digital outputs

4.3.1 Task:

1. Connect the DC motor to Digital Output D7 and D6.
2. Write the program and check all the combinations of digital outputs; 00, 01, 10 and 11. First combination is shown in prog. 1

Program 1: DC Motor Control with Digital Outputs.

```

1  void setup()
2  {
3      pinMode(7, OUTPUT);
4      pinMode(6, OUTPUT);
5      // D7=0, D6=0
6      digitalWrite(7, LOW);
7      digitalWrite(6, LOW);
8      delay(3000);
9      // Write other combinations here...
10
11 }
12 void loop()
13 {
14
15 }
```

3. For each combination of digital outputs mark the state of the motor (fulfill the tbl. 1).

Table 1: All combinations of the states of motor's connectors.

| D7 | D6 | Motor rotation |
|----|----|----------------|
| 0 | 0 | |
| 0 | 1 | |
| 1 | 0 | |
| 1 | 1 | |

4.3.2 Questions:

2. Try to stop the shaft of the DC motor for a short time and try to remember how difficult it is?
3. Why does motors' shaft not spinning if the digital output state are 1 and 1.

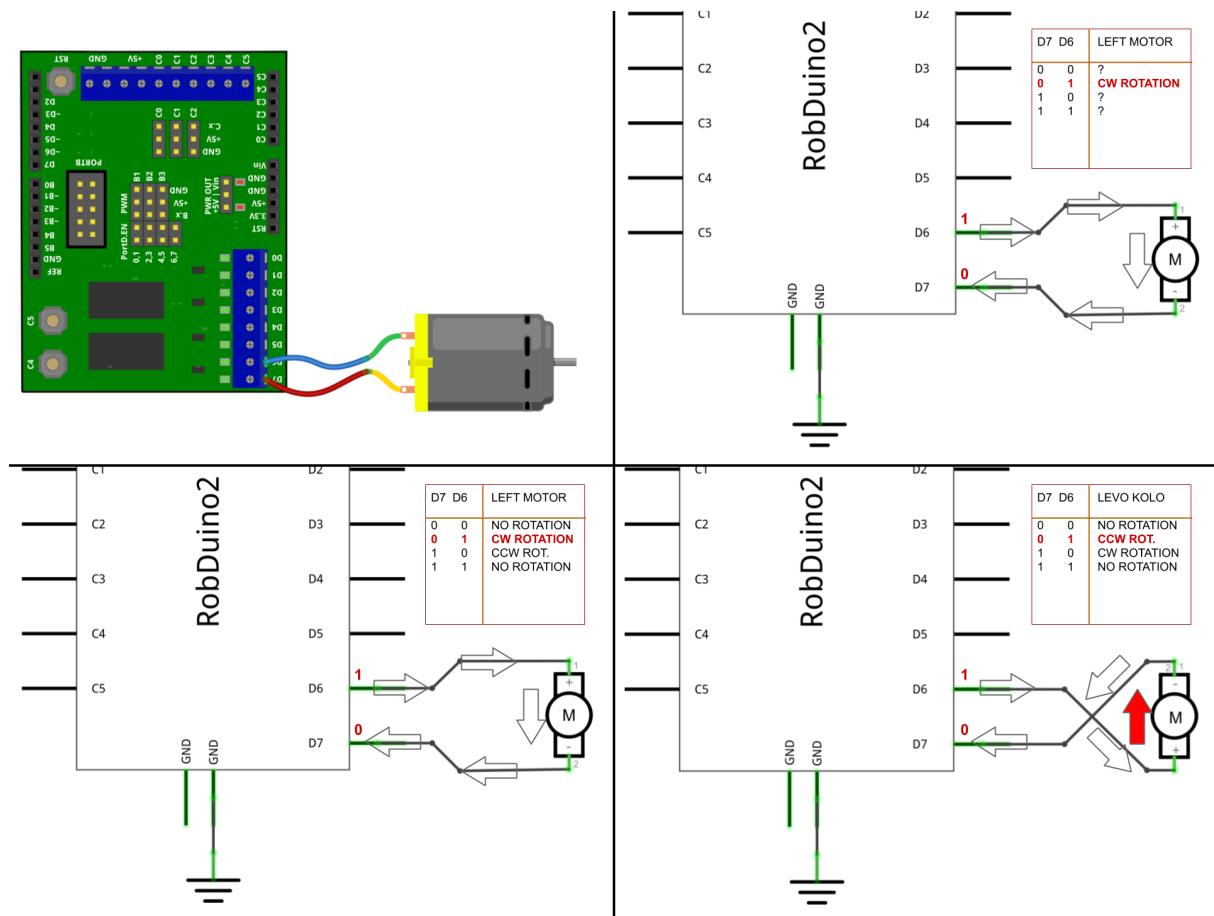


Figure 1: Wiring the DC motor to controller.

4.3.3 Summary

The motor's shaft is spinning according to the direction of the electric current through the motor. The torque is weak.

4.3.4 Issues